



KFUPM

ICS233 PROJECT REPORT

Group#4

Single Cycle and Pipelined Processor

Team Members Names
(L)HASSAN ALSABBAGH
RIDHA ALAWAMI
MOHAMMED ALJARAD

Contents


1. Design and Implementation.....	2
a. Design detailed description	2
b. Component circuits drawings	2
i. Register File.....	2
ii. ALU	3
iii. Logical Unit.....	3
iv. Shifter.....	4
v. AU.....	4
vi. LU and Shifter.....	5
vii. Main controller	5
viii. PC	6
ix. Next PC.....	6
x. CPU(data path).....	7
xi. NPC.....	7
xii. P2	8
xiii. P3	8
xiv. Ex MEM WB.....	9
xv. HAZARD DETECT AND FORWARD	10
c. Complete description of the control logic and control signals with a table and logic equations.....	11
i. Signals control table.....	11
ii. Logic equations	12
d. Description of the forwarding logic, and the logic implemented in stalling.....	12
2. Simulation and Testing Programs	13
a. Number of ones in a register	13
b. Selection sort procedure:.....	14
c. Remaining untested instructions:	15
3. Teamwork	17
i. Design and Implementation, simulation and testing, design and results reporting	17
ii. Execution plan.....	17
iii. Meetings	18

1. Design and Implementation


a. Design detailed description

b. Component circuits drawings


i. Register File

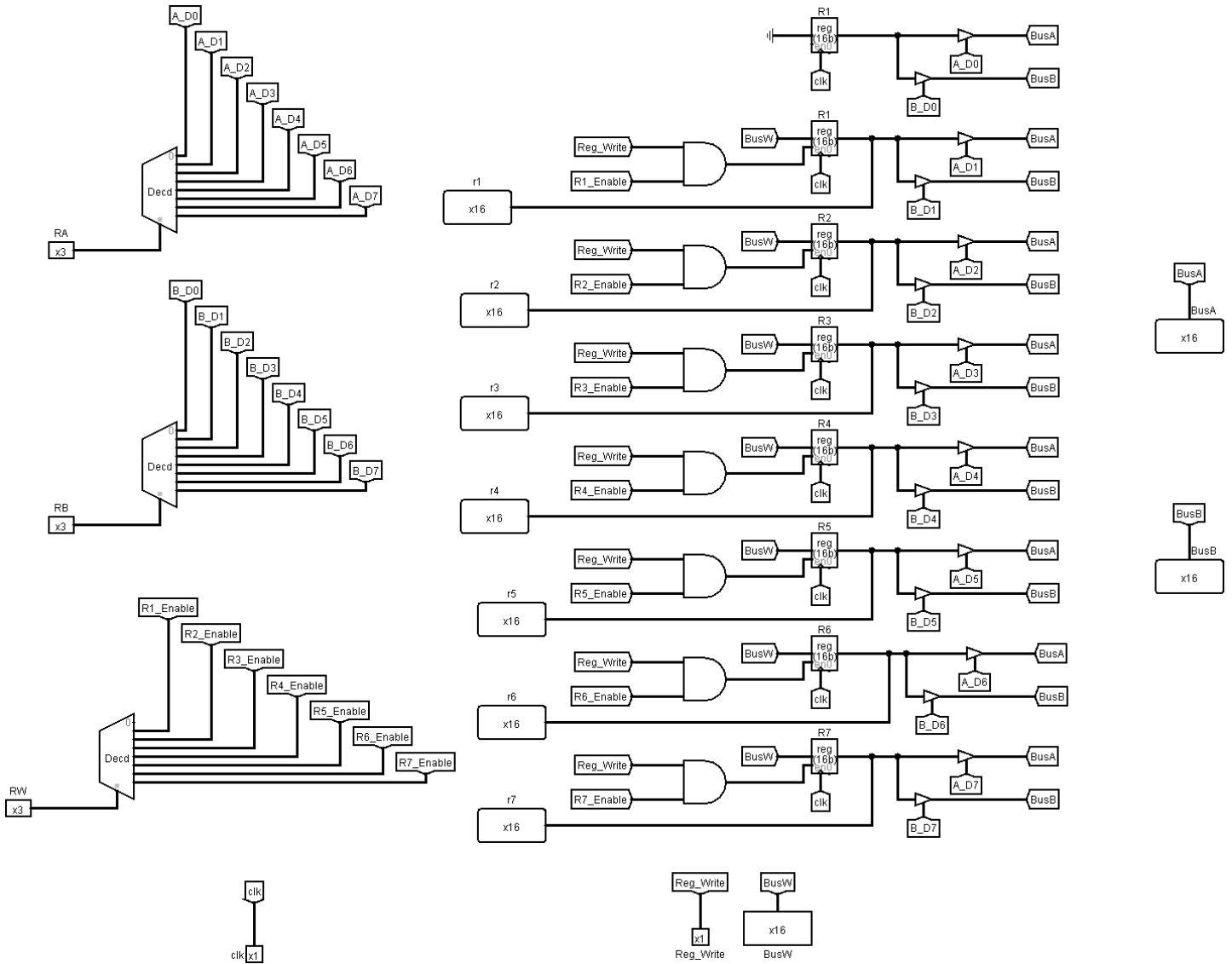


ii. ALU

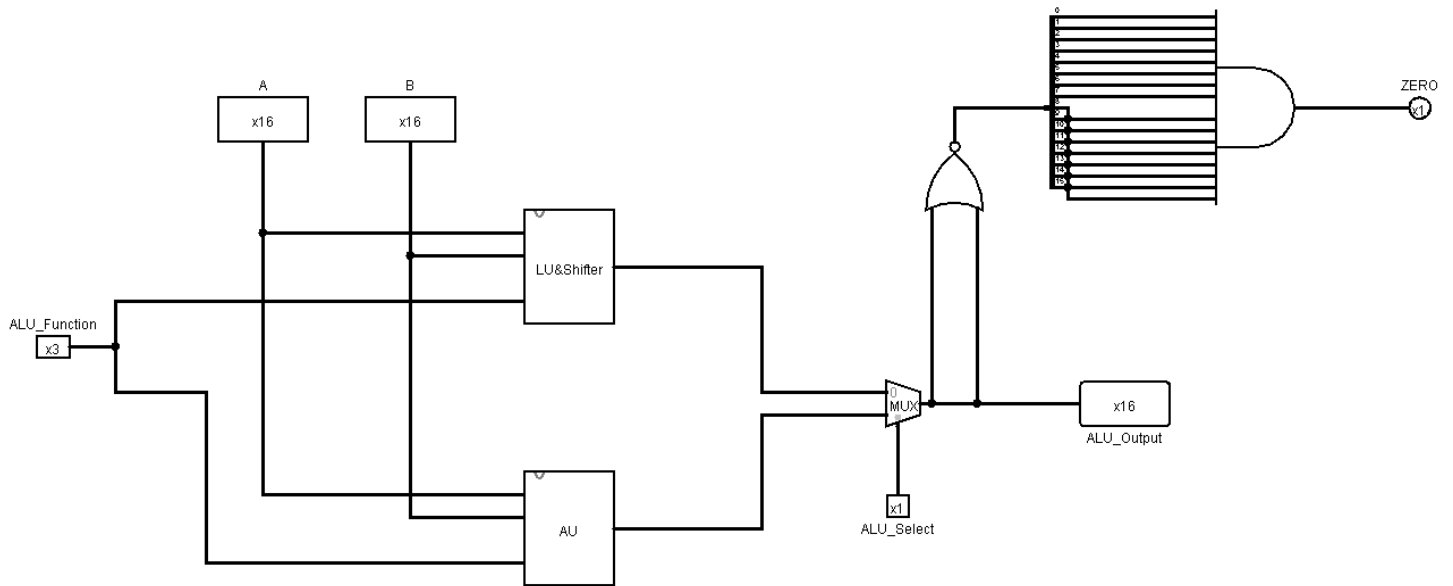


iii. Logical Unit

 


iv. Shifter

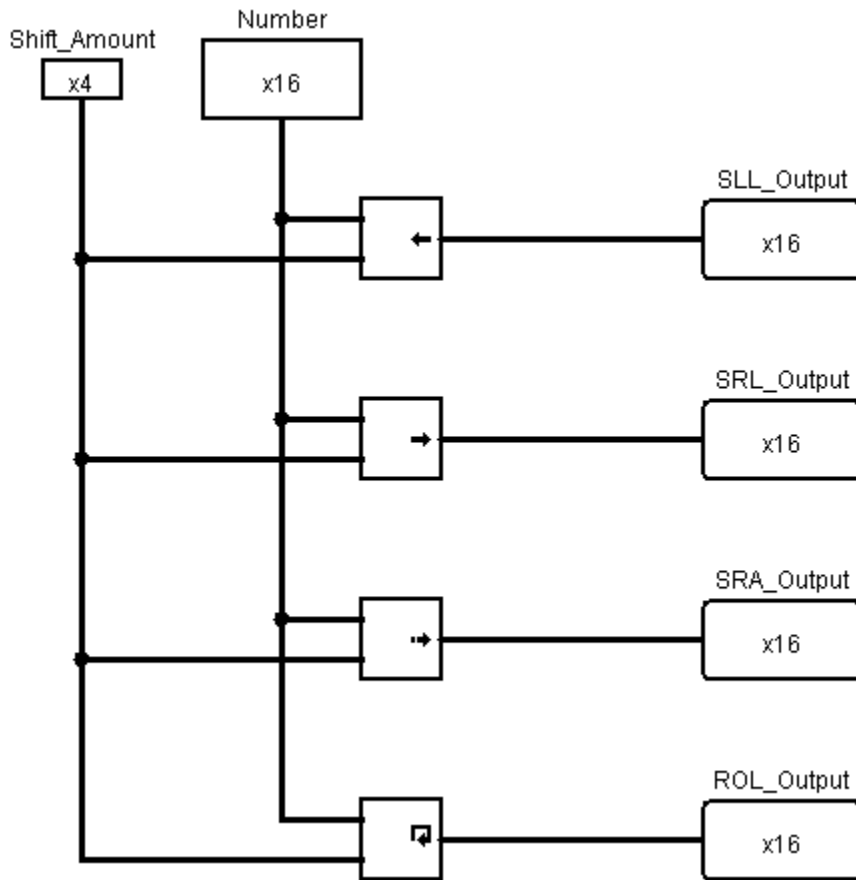


v. AU

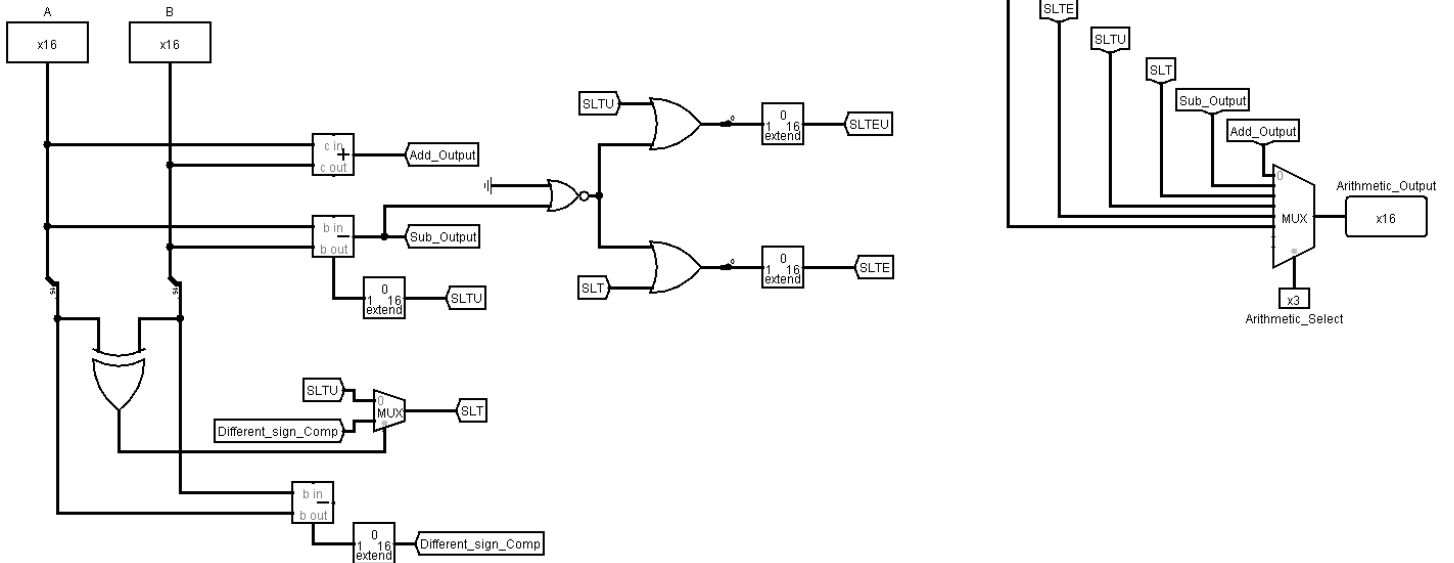


vi. LU and Shifter

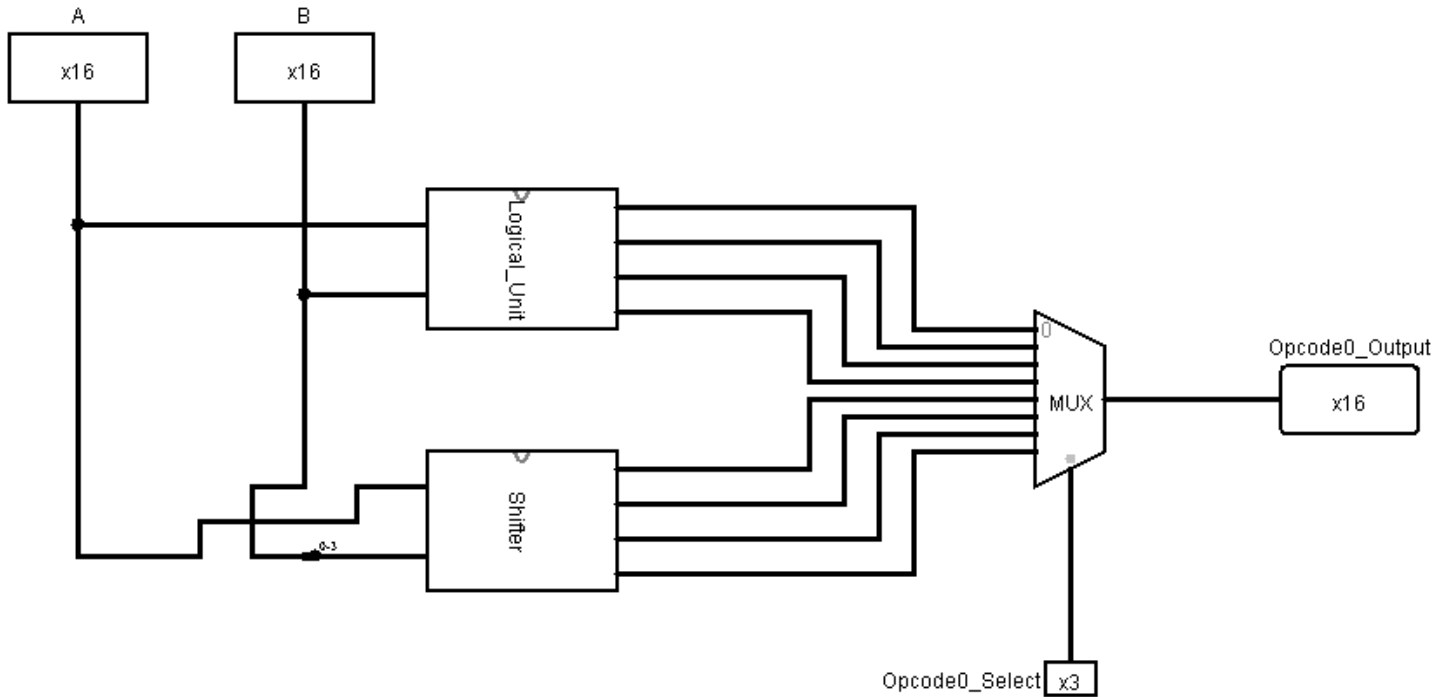


vii. Main controller

 


viii. PC

 


ix. Next PC

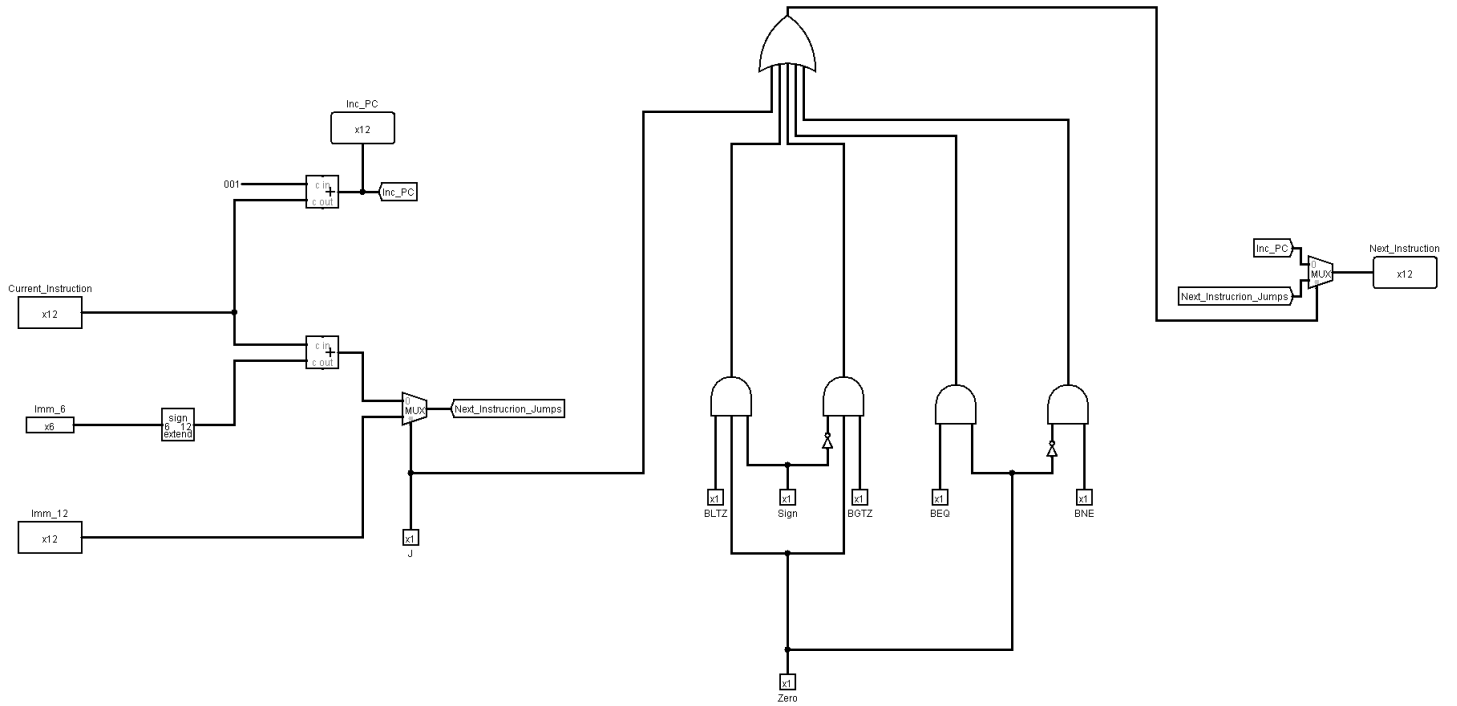


x. CPU(data path)

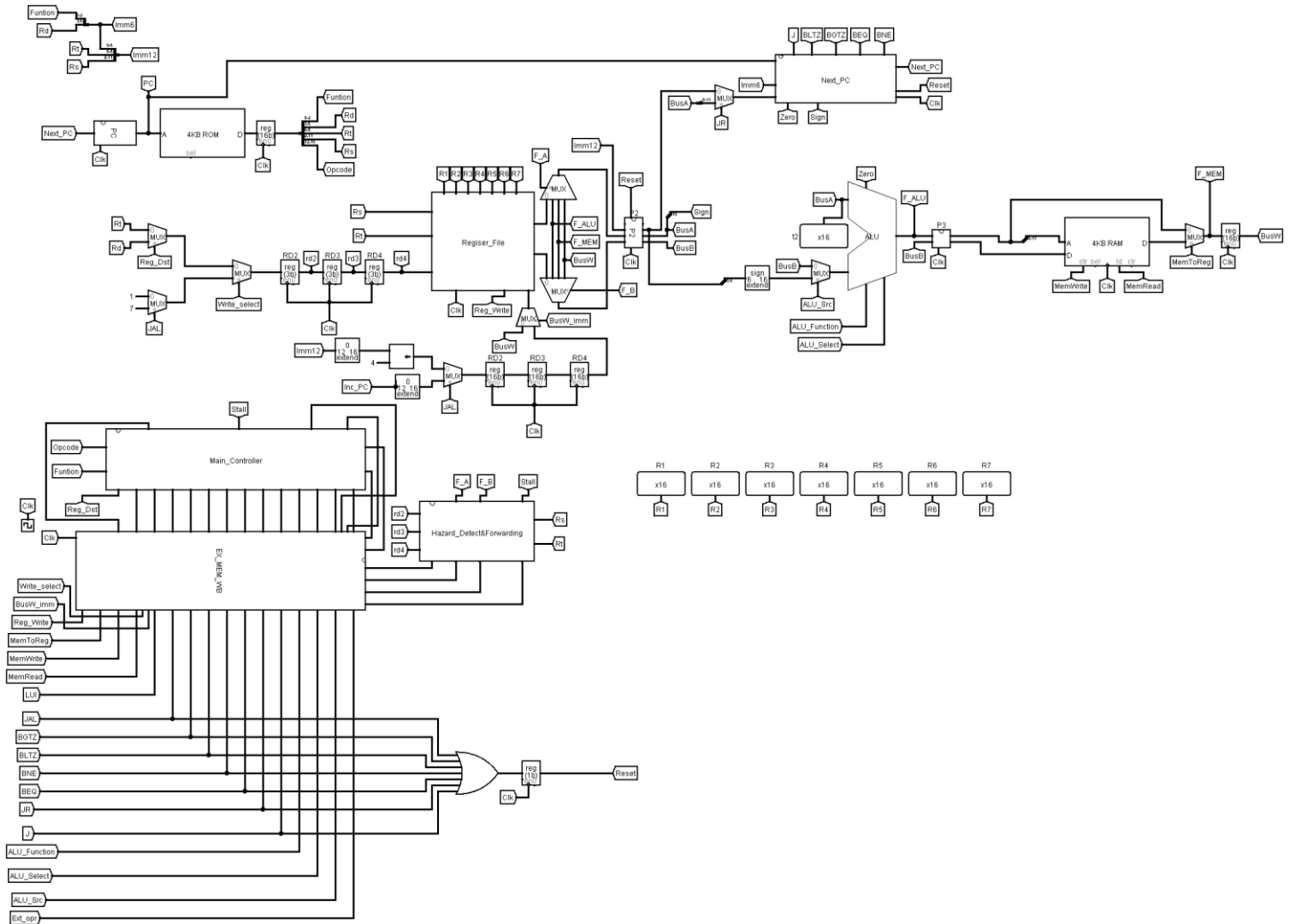


xi. NPC

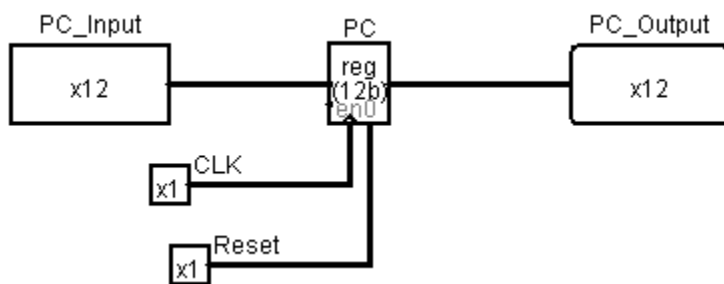


xii. P2

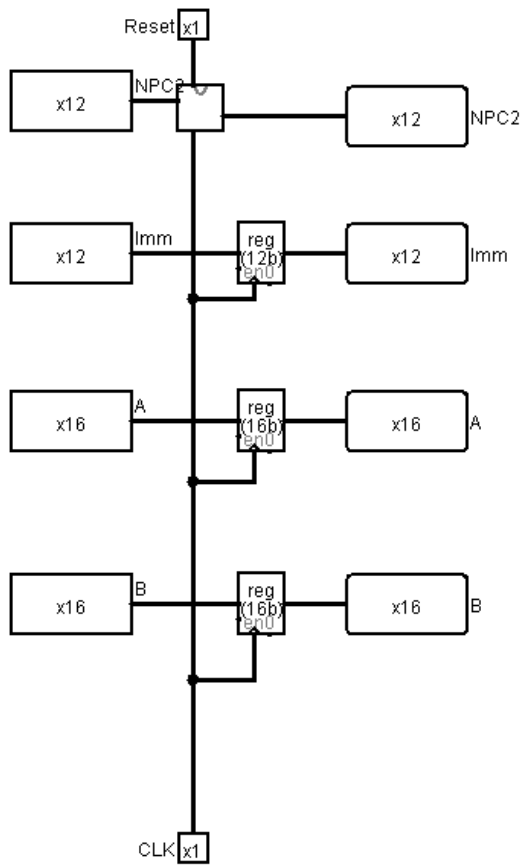


xiii. P3

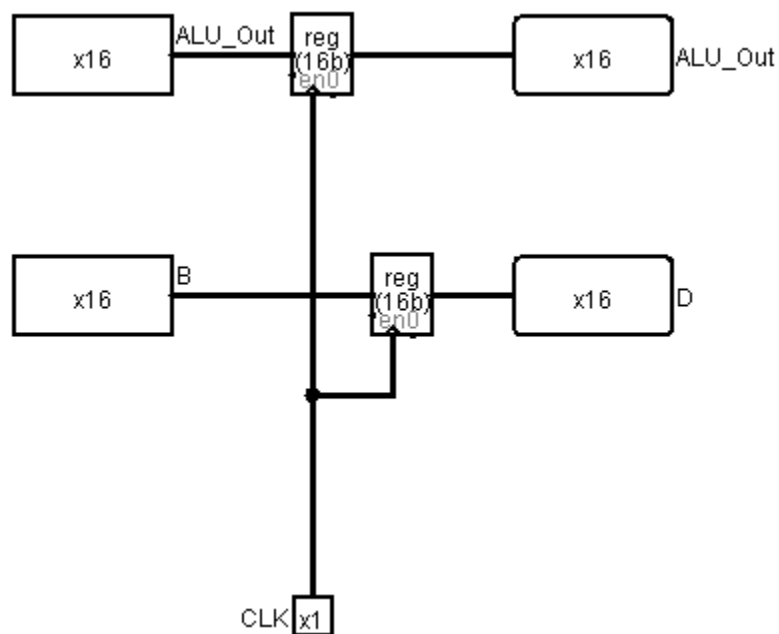

xiv. Ex MEM WB

 

xv. HAZARD DETECT AND FORWARD

 

c. Complete description of the control logic and control signals with a table and logic equations

i. Signals control table

Op	Reg Dst	Reg Write	Ext Op	ALU Src	ALU Op	Beq	Bne	BGZ	BLZ	J	JAL	LUI	Mem Read	Mem Write	Mem toReg	ALU Select
R-type	1 = Rd	1	x	0=BusB	R-type	0	0	0	0	0	0	0	0	0	0	x
lw	0 = Rt	1	1=sign	1=Imm	ADD	0	0	0	0	0	0	0	1	0	1	1
sw	x	0	1=sign	1=Imm	ADD	0	0	0	0	0	0	0	0	1	x	1
beq	x	0	x	0=BusB	SUB	1	0	0	0	0	0	0	0	0	x	1
bne	x	0	x	0=BusB	SUB	0	1	0	0	0	0	0	0	0	x	1
andi	0 = Rt	1	0=zero	1=Imm	AND	0	0	0	0	0	0	0	0	0	0	0
ori	0 = Rt	1	0=zero	1=Imm	OR	0	0	0	0	0	0	0	0	0	0	0
addi	0 = Rt	1	1=sign	1=Imm	ADD	0	0	0	0	0	0	0	0	0	0	1
j	x	0	x	x	x	0	0	0	0	1	0	0	0	0	x	0
jr	x	0	x	x	x	0	0	0	0	1	0	0	0	0	0	0
lui	x	1	x	1=Imm	SLL	0	0	0	0	0	0	1	0	0	0	1
jal	x	1	x	x	x	0	0	0	0	0	1	0	0	0	x	0
jalr	x	1	0	0	x	0	0	0	0	1	1	0	0	0	0	0
bltz	x	0	x	0=BusB	SUB	0	0	0	1	0	0	0	0	0	x	1
blez	x	0	x	0=BusB	SUB	1	0	0	1	0	0	0	0	0	x	1
Bgtz	x	0	x	0=BusB	SUB	0	0	1	0	0	0	0	0	0	x	1
Bgez	x	0	x	0=BusB	SUB	1	0	1	0	0	0	0	0	0	x	1

ii. Logic equations

Reg Dst \leq **R-type**

Reg Write \leq **R-type** + **lw** + **sw** + **andi** + **ori** + **addi** + **jal** + **lui**

Ext Op \leq **lw** + **sw** + **addi**

ALU_Src \leq **lw** + **sw** + **andi** + **ori** + **addi**

BEQ \leq **beq** + **blez** + **bgez**

BNE \leq **bne**

BGTZ \leq **bgtz** + **bgez**

BLTZ \leq **bltz** + **blez**

Mem Read \leq **lw**

Mem Write \leq **sw**

Mem to Reg \leq **lw**

ALU Select \leq **R-type** + **lw** + **sw** + **beq** + **bne** + **addi** + **lui** + **bgtz** + **bgez** + **blez** + **bltz**

LUI \leq **lui**

JAL \leq **jalr** + **jal**

J \leq **jr** + **jal** + **j**

d. Description of the forwarding logic, and the logic implemented in stalling forwarding logic:

first we check for dependencies in rd, or rt, then if there is a dependency we take the rd or rt value from that stage, then the value is forwarded.

stalling logic:

if there is any jump related instruction (j, branch), we save its address until we reach the ALU stage, then we jump and hold the other instructions for a certain cycles delay, after that we continue executing the instructions.

2. Simulation and Testing Programs

a. Number of ones in a register

This test's purpose is to count the number of ones of a given number in binary.

First adding the number to register \$2 and the shift amount in \$1

```
addi $2,$0,31
```

```
addi $1, $1, 1
```

then compare the value to less than zero in register \$5 and start the loop label here

```
slt $5, $0, $2
```

then set the loop condi. to exit when the number equals 0

```
beq $5, $0 ,7
```

then see if the first bit is 1 or not by anding it with 1

```
andi $3,$2,0x01
```

and then add the result of anding to register \$7

```
add $7,$3,$7
```

finally shift right logical of the number and jump back to loop

```
srl $2,$2,1
```

```
j loop
```

inputs:31

expected output:5

#	instruction	Binary	Hexadecimal
1.	addi \$2,\$0,31	1000 000 010 011111	809F
2.	addi \$1, \$1, 1	1000 001 001 000001	8241
	loop		
3.	slt \$5, \$0, \$2	0001 000 010 101010	10AA
4.	beq \$5, \$0 , 8	0100 101 000 001000	4A08
5.	andi \$3,\$2,0x01	0110 010 011 000001	64C1
6.	add \$7,\$3,\$7	0001 011 111 111000	17F8
7.	srl \$2,\$2,1	0000 010 001 010101	0455
8.	j loop	1001 000 000 000010	9002

b. Selection sort procedure:

The purpose of this program is to sort an array of 8 words read from the memory.

inputs: 8 words from the memory

expected output: sorted the 8 words in ascending order.

#	Instruction	Bin	Hex
1	addi \$2, \$2, 7	1000 010 010 000 111	8487
2	add \$7, \$2, \$0	0001 010 000 111 000	1438
	Outer Loop		
3	xor \$1, \$1, \$1	0000 001 001 001 011	024b
4	beq \$2, \$1, 31	0100 010 001 011 111	445F
5	add \$6, \$0, \$2	0001 000 010 110 000	10b0
	Inner Loop		
6	beq \$1, \$2, 10	0100 001 010 001 010	428a
7	lw \$7, 0(\$6)	0010 110 111 000 000	2dc0
8	lw \$3, 0(\$1)	0010 001 011 000 000	22c0
9	slt \$4, \$3, \$7	0001 011 111 100 010	17e2
10	blez \$4, 3	1101 100 000 000 011	d803
11	addi \$1, \$1, 1	1000 001 001 000 001	8241
12	j 5	1001 000 000 000 110	9005
	Update Max		
13	add \$6, \$0, \$1	0001 000 001 110 000	1070
14	addi \$1, \$1, 1	1000 001 001 000 001	8241
15	j 5	1001 000 000 000 110	9005
	Swap		
16	lw \$3, 0(\$2)	0010 010 011 000 000	24c0
17	lw \$7, 0(\$6)	0010 110 111 000 000	2dc0
18	sw \$7, 0(\$2)	0011 010 111 000 000	35c0
19	sw \$3, 0(\$6)	0011 110 011 000 000	3cc0
20	addi \$2, \$2, -1	1000 010 010 111 111	84bf
21	j 2	1001 000 000 000 011	9002

c. Remaining untested instructions:

1. AND, OR, NOR

Purpose is to test and, or, nor with the numbers 5 and 6

Input: 5 into register 2, and 6 into register 3

Expected output:

#	Instruction	Bin	Hex
1	addi \$2, \$2, 5	1000 010 010 000 101	8485
2	addi \$3, \$3, 6	1000 011 011 000 110	86C6
3	and \$1, \$2, \$3	0000 010 011 001 000	04C8
4	or \$4, \$2, \$3	0000 010 011 100 001	04E1
5	nor \$5, \$2, \$3	0000 010 011 101 010	04EA

2. SLL, SRA, ROL

Purpose to test sll, sra, rol with the numbers 5 and 6

#	instruction	bin	hex
1	addi \$1, \$1, 1	1000 001 001 000 001	8241
2	addi \$2, \$2, 5	1000 010 010 000 101	8485
3	sll \$3, \$2, \$1	0000 010 001 011 100	045C
4	srl \$4, \$2, \$1	0000 010 001 100 101	0465
5	sra \$5, \$2, \$1	0000 010 001 101 110	046E
6	rol \$6, \$2, \$1	0000 010 001 110 111	0477

3. SUB, SLTU, SLTE, SLTEU, JR

Purpose is to test sub, sltu, slte, slteu, and jr with the numbers 5 and 6

Input: 5 in register 2, and 6 in register 3

Expected output:

Result of sub = 1 in register 5

Result of slt = 1 in register 6

Result of sltu = 1 in register 7

Result of slte = 1 in register 4

jr will jump to address 1

#	Instruction	bin	hex
1	addi \$1, \$1, 5	1000 001 001 000 101	8245
2	addi \$2, \$2, 5	1000 010 010 000 101	8485
3	addi \$3, \$3, 6	1000 011 011 000 110	86C6
4	sub \$5, \$3, \$2	0001 011 010 101 001	16A9
5	slt \$6, \$2, \$3	0001 010 011 110 010	14F2
6	sltu \$7, \$2, \$3	0001 010 011 111 011	14FB
7	slte \$4, \$2, \$1	0001 010 001 100 100	1464
8	JR 1	0001 000 000 001 110	100E

4. ORI, BNE, JALR

Purpose is to test ori, bne, jalr with the numbers 5 and 7 and bne wont branch, jalr will jump.

Input: 5 in register 2, and 7 in register 3

Expected output: ori 3 and 7 => 7

#	instruction	bin	hex
1	addi \$2, \$2, 5	1000 010 010 000 101	8485
2	andi \$3, \$2, 7	0110 010 011 000 111	64C7
3	ori \$4, \$3, 3	0111 011 100 000 011	7703
4	bne \$1, \$3, 8	0101 001 011 001 000	52C8
5	jalr \$2, \$1	0001 001 000 010 111	1217

5. BLTZ, BLEZ

Purpose is to test bltz and blez with the number zero, bltz won't branch, blez will branch to address 7

#	instruction	bin	hex
1	bltz \$0, 7	1100 000 000 000 111	C007
2	blez \$0, 7	1101 000 000 000 111	D007

6. BGTZ, BGEZ

Purpose to test bgtz, and bgez with number zero bgtz won't branch, bgez will branch to address 7

#	instruction	bin	hex
1	bgtz \$0, 7	1110 000 000 000 111	E007
2	bgez \$0, 7	1111 000 000 000 111	F007

7. JAL, LUI


Purpose is to test jal and lui, jal will jump to address 3, and lui assuming it is at address 3 will load upper immediate the value 5 into register 1.

#	instruction	bin	hex
1	jal 3	1011 000 000 000 011	B003
2	lui 5	1010 000 000 000 101	A005

3. Teamwork

- i. Design and Implementation, simulation and testing, design and results reporting

scale of 9 points shared on 3 members.

 

- ii. Execution plan

#	Task		
Week	Design and Implementation	simulation and testing	design and results reporting
10	Dividing tasks	-	-
11	The register file, ALU	-	-
12	Instruction Memory, Data Memory	number of 1's in a register	write the report
13	PC, Next PC, MC, ALUctrl, Datapath In short finish up the single processor	Selection sort procedure, Max procedure, tests each of the remaining untested instructions	Testing's, write the report.
14	Pipelined processor	-	write the report
15	Pipelined processor Implementing forwarding, and stalls. In short finish up the pipeline processor	Testing the pipeline correctness	Finish the report

iii. Meetings

#	Topics discussed	Date and Time
1	Design	11/22/17 2-4 PM
2	Design	11/29/17 2-3 PM
3	Design, implementation, testing	12/6/17 2-6 PM
4	Design, implementation, testing	12/10/17 6-8 PM
5	Design, implementation, testing	12/12/17 8-12PM
6	Design, implementation, testing	12/14/17 2-11:30 PM
7	Pipeline Design and implementation	12/20/17 2:10-5 PM
8	Pipeline Design and implementation	12/26/17 1:30-7:30 PM
9	Pipeline Design and implementation	12/27/17 2-9 PM